

Dynamic Switching

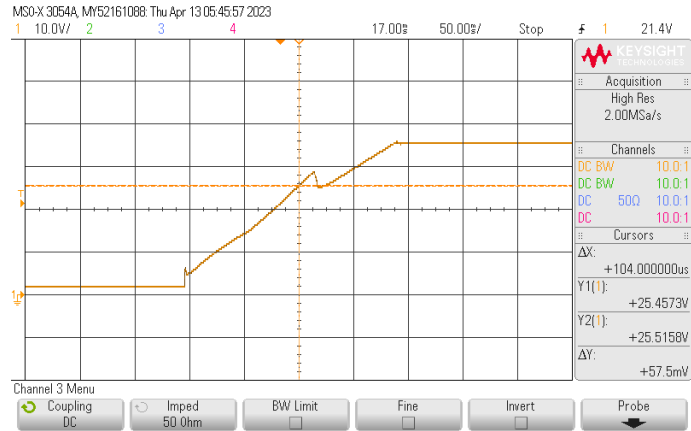


Figure 1: Turning On Low Voltage

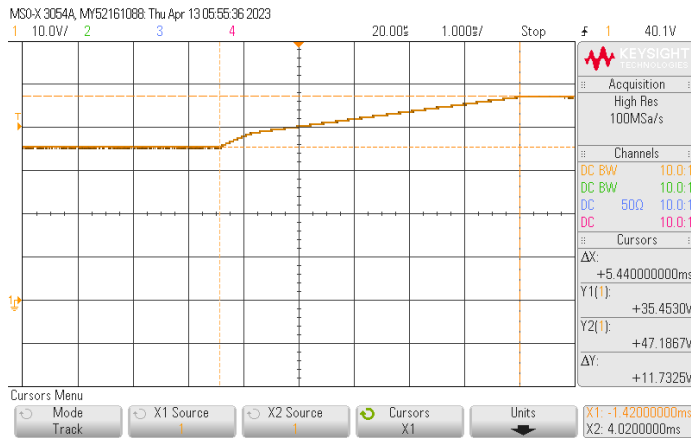


Figure 2: Engaging High Voltage

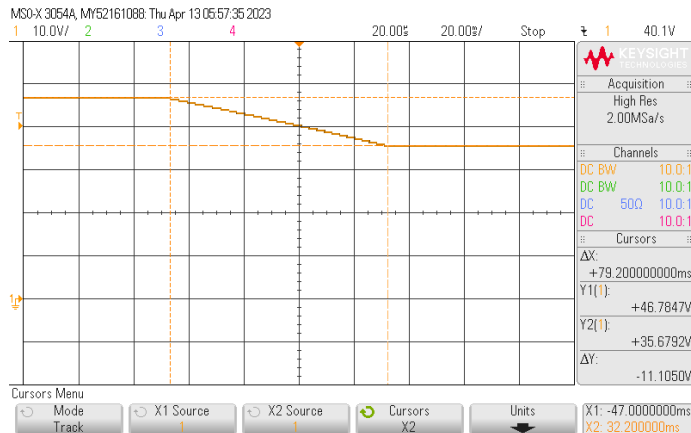


Figure 3: Disengaging High Voltage